

**Question 2****(6 marks)**

A tram is powered by four identical electric motors. Each motor has a maximum power output of 30.0 kW. The motors are connected in parallel and powered by  $6.00 \times 10^2$  V DC from overhead power lines. When the motors are operating at maximum power output there is a back emf of  $5.20 \times 10^2$  V with an internal resistance of 1.39  $\Omega$ .

- (a) Calculate the current drawn by each motor when operating at maximum power output. (4 marks)

Answer \_\_\_\_\_ A

- (b) After operating for a while one of the motors becomes jammed. Describe, with a reason, what happens to the current in that motor when it becomes jammed. (2 marks)

---

---

---

---