	For copyright reasons this image cannot be reproduced in the online version of this document, but may be viewed at the link listed on the acknowledgements page.
-	
(i)	Draw an arrow showing the direction of the flow of conventional curre circuit.
(i) (ii)	

\_\_\_\_N